

La cascoded Amp calculations -

$$I_2 = \frac{Pdispp}{Voo} = \frac{1 \times 10^{-3}}{1.8} = 556 U A$$

$$1.7 = 1.8 - \sqrt{\frac{2 \times 100}{61.4 - (W|L)_3}}$$
 regal gum and (W)L)

$$(0.1)^2 = \frac{3.25}{(\omega/L)_3} = .01$$

$$=$$
 $(\omega | L)_3 = 325.75289 = (\omega | L)_4$

$$3 \quad Av = \frac{9m_1}{9ds_3} = \sqrt{\frac{2\beta_1}{\lambda_p}} \times \frac{1}{\lambda_p}$$

$$(-70)^2 \times (.09)^2 = 2 \times 122.8 \text{ (w/L)}$$

6

$$0.6 - \sqrt{\frac{2 \times 100}{122.8 \times 16.16}} = \sqrt{\frac{27}{\beta_2}}$$

$$(6.2825)^2 = .08 = 2 \times 100$$
 $122.8 \times (\omega/L)_2$

(*) 6) we will also find Vin de bias value to accurately get gain required -

$$V_{in} = V_{th} + V_{0N}$$

$$= 0.4 + \sqrt{\frac{2 \times 100}{122.8 \times 16.16042}}$$









